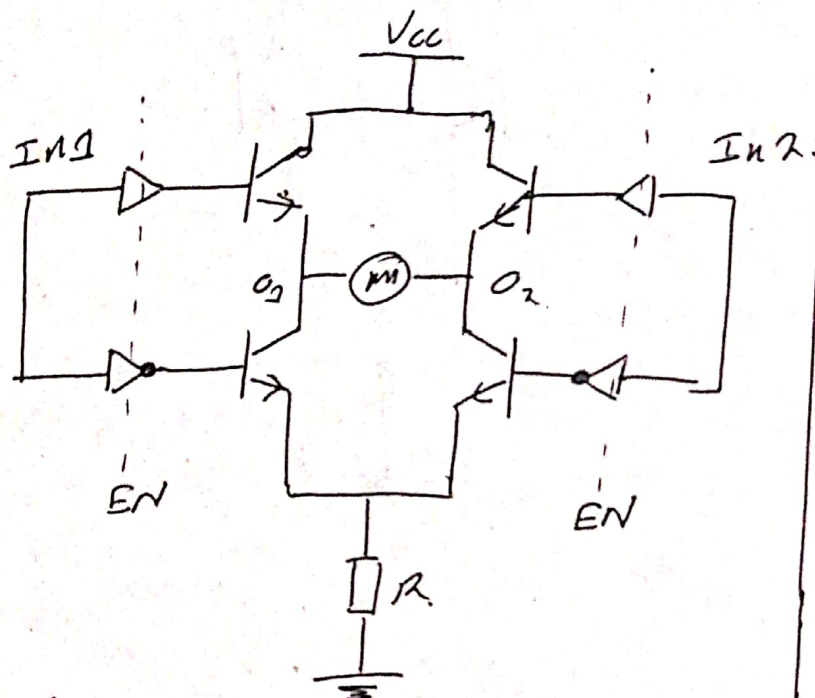


# Assignment 03

190301 H

\* A single H bridge can be represented as,



→ For this circuit I Assume the BJTs are Si

→ Fwd BE  $\Rightarrow 0.7V$

→  $V_{CE_{sat}} \rightarrow 0.2V$

When one of  $In$  is High.  $\frac{1}{2}V_L$

$$V_{cc} = 2 \times 0.2 + V_m + IR$$

$$\therefore V_m = (V_{cc} - IR - 0.4)$$

\* Since Motor is Not connected  $I \rightarrow 0$

\* Consider  $4.8V \rightarrow \text{logic } 1$   
(5V)

$0.2V \rightarrow \text{logic } 0$   
(0V)

EN	In1	In2	Out1	Out2
0	0	0	Z	Z
0	0	1	Z	Z
0	1	0	Z	Z
0	1	1	Z	Z
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1
PWM	0	1	0	1
PWM	1	0	1	0

} High Impedance state

← Coasting

← Current(I) flows  $out1 \rightarrow out2$

← Cur(I) flows  $out2 \rightarrow out1$

← Bracking

← I flows  $03 \rightarrow 02$  } with speed control  
← I flows  $02 \rightarrow 01$